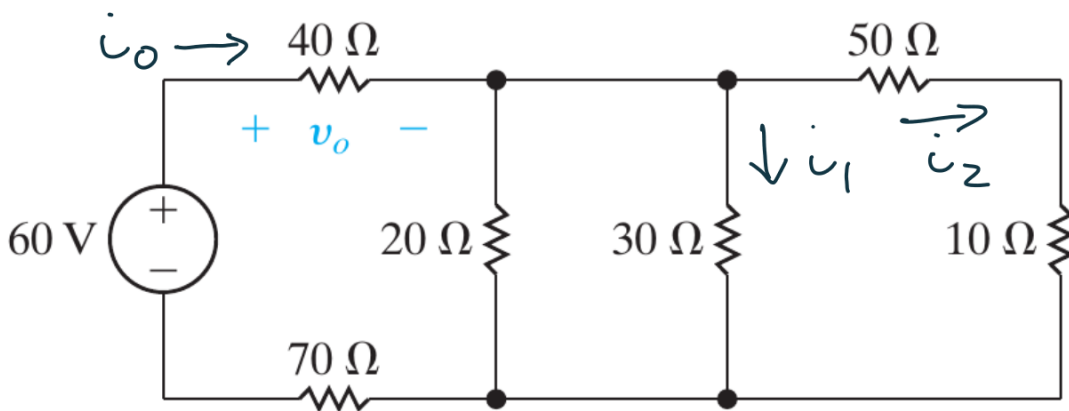


### Assessment Problem 3.4

- Use voltage division to determine the voltage  $v_o$  across the  $40\ \Omega$  resistor in the circuit shown.
- Use  $v_o$  from part (a) to determine the current through the  $40\ \Omega$  resistor, and use this current and current division to calculate the current in the  $30\ \Omega$  resistor.
- How much power is absorbed by the  $50\ \Omega$  resistor?



$$\begin{aligned} \text{(a)} \quad R_{eq} &= 40 + 20 \parallel 30 \parallel (50 + 10) + 70 \\ &= 110 + \frac{1}{\frac{1}{20} + \frac{1}{30} + \frac{1}{60}} \\ &= 120\ \Omega \end{aligned}$$

$$\therefore v_o = \frac{40}{120} \times 60 = 20\ \text{V}$$

$$\text{(b)} \quad i_o = \frac{v_o}{40} = 0,5\ \text{A}$$

$$R_{eq} = 20 \parallel 30 \parallel (50 + 10) = 10\ \Omega$$

$$\therefore i_1 = \frac{10}{30} \times 0,5 = 166,67\ \text{mA}$$

$$(c) \quad i_2 = \frac{10}{60} \times 0,5 = 83,3 \text{ mA}$$

$$P_{50\Omega} = i_2^2 \times 50 = 347,22 \text{ mW}$$

